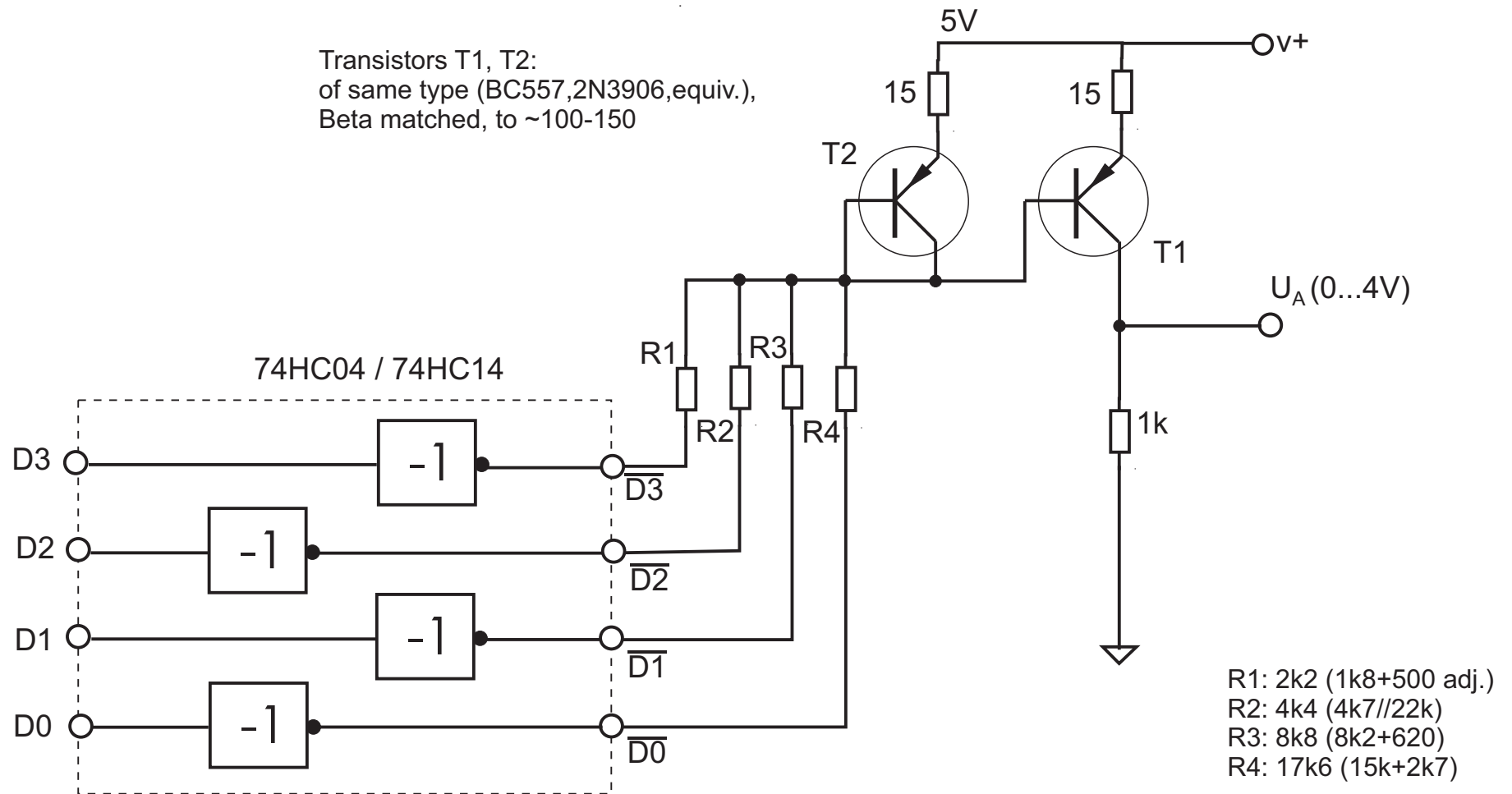




application: e.g. show a counter's progress
on an oscilloscope as stair-trace

Prof.Dr. Manfred Hamann
University of Applied Science Wolfenbuettel

Date/ Revision	Title	page
v. 02/ 201905	low-cost 4 bit D/A Converter	1 of 1